



UNIVERSITY OF MASSACHUSETTS
Dept. of Electrical & Computer Engineering

Digital Computer Arithmetic
ECE 666

Part 6b
High-Speed Multiplication - II

Israel Koren

ECE666/Koren Part.6b.1

Copyright 2010 Koren

Accumulating the Partial Products


- ◆ After generating partial products either directly or using smaller multipliers
- ◆ Accumulate these to obtain final product
 - * A fast multi-operand adder
- ◆ Should take advantage of particular form of partial products - reduce hardware complexity
- ◆ They have fewer bits than final product, and must be aligned before added
- ◆ Expect many columns that include fewer bits than total number of partial products - requiring simpler counters

ECE666/Koren Part.6b.2


Copyright 2010 Koren

 Example - Six Partial Products

- ◆ Generated when multiplying unsigned 6-bit operands using one-bit-at-a-time algorithm
- ◆ 6 operands can be added using 3-level carry-save tree



 
- ◆ Number of (3,2) counters can be substantially reduced by taking advantage of the fact that all columns but 1 contain fewer than 6 bits
- ◆ Deciding how many counters needed - redraw matrix of bits to be added:




ECE666/Koren Part.6b.3

Copyright 2010 Koren

 
Reduce Complexity - Use (2,2) Counters (HAs)




(a) Level 1 carry-save addition.

 

(c) Level 2 carry-save addition.

 

(b) Results of level 1.

 

(d) Level 3 carry-save addition.

- ◆ Number of levels still 3, but fewer counters


ECE666/Koren Part.6b.4

Copyright 2010 Koren

Further reduction in number of counters


◆ Reduce # of bits to closest element of 3,4,6,9,13,19,...

 ◆ 15 (3,2) and 5 (2,2) vs. 16 (3,2) and 9 (2,2) counters



(a) Level 1 carry-save addition.

(c) Level 2 carry-save addition.

 


(b) Results of level 1.

 (d) Level 3 carry-save addition.

Modified Matrix for Negative Numbers

- ◆ Sign bits must be properly extended
- ◆ In row 1: 11 instead of 6 bits, and so on
- ◆ Increases complexity of multi-operand adder
- ◆ If two's complement obtained through one's complement - matrix increased even further



Reduce Complexity Increase

- ◆ Two's complement number

S S S S S S Z₄ Z₃ Z₂ Z₁ Z₀
with value

$$-s \cdot 2^{10} + s \cdot 2^9 + s \cdot 2^8 + s \cdot 2^7 + s \cdot 2^6 + s \cdot 2^5 + z_4 \cdot 2^4 + z_3 \cdot 2^3 + z_2 \cdot 2^2 + z_1 \cdot 2^1 + z_0$$

- ◆ Replaced by

0 0 0 0 0 (-s) Z₄ Z₃ Z₂ Z₁ Z₀

- ◆ since

$$\begin{aligned} & -s \cdot 2^{10} + s \cdot (2^9 + 2^8 + 2^7 + 2^6 + 2^5) \\ & = -s \cdot \mathfrak{S}_{10} + s \cdot (\mathfrak{S}_{10} - \mathfrak{S}_2) = -s \cdot \mathfrak{S}_2 \end{aligned}$$

New Bit Matrix

- ◆ To get **-s** in column **5** - complement original **s** to **(1-s)** and add **1**

* Carry of **1** into column **6** serves as the extra **1** needed for sign bit of second partial product

10	9	8	7	6	5	4	3	2	1	0
					1					
					$\overline{s_1}$	o	o	o	o	o
					$\overline{s_2}$	o	o	o	o	o
					$\overline{s_3}$	o	o	o	o	o
					$\overline{s_4}$	o	o	o	o	o
					$\overline{s_5}$	o	o	o	o	o
					$\overline{s_6}$	o	o	o	o	o

- ◆ New matrix has fewer bits but higher maximum height (**7** instead of **6**)

Eliminating Extra 1 in Column 5

- ◆ Place two sign bits s_1 and s_2 in same column
- ◆ $(1-s_1)+(1-s_2) = 2 -s_1 -s_2$
- ◆ 2 is carry out to next column
- ◆ Achieved by first extending sign bit s_1

10	9	8	7	6	5	4	3	2	1	0
				$\overline{s_1}$	s_1	o	o	o	o	o
				$\overline{s_2}$	o	o	o	o	o	
			$\overline{s_3}$	o	o	o	o	o		
		$\overline{s_4}$	o	o	o	o	o			
	$\overline{s_5}$	o	o	o	o	o				
	$\overline{s_6}$	o	o	o	o	o				

ECE666/Koren Part.6b.9

Copyright 2010 Koren

Using One's Complement and Carry

- ◆ Add extra carries to matrix
- ◆ Full circles - complements of corresponding bits are taken whenever $s_i=1$
- ◆ Extra s_6 in column 5 increases maximum column height to 7

- ◆ If last partial product is always positive (i.e., multiplier is positive) - s_6 can be eliminated

10	9	8	7	6	5	4	3	2	1	0
				$\overline{s_1}$	s_1	•	•	•	•	•
				$\overline{s_2}$	•	•	•	•	•	s_1
			$\overline{s_3}$	•	•	•	•	•	s_2	
		$\overline{s_4}$	•	•	•	•	•	s_3		
	$\overline{s_5}$	•	•	•	•	•	s_4			
	$\overline{s_6}$	•	•	•	•	•	s_5			
					s_6					

ECE666/Koren Part.6b.10

Copyright 2010 Koren

Example 2: Using radix-4 modified Booth's

◆ Same recoded multiplier $010\bar{1}0\bar{1}$

9	8	7	6	5	4	3	2	1	0
		0	1	1	0	1	0	1	0
	1	0	0	1	0	1	0		
1	1	0	1	1	0				
0	0	1	1	1	1	0	0	1	0

9	8	7	6	5	4	3	2	1	0
		0	1	1	0	1	0	0	1
	1	0	0	1	0	0	1		1
1	1	0	1	1	0		1		
					0				
0	0	1	1	1	1	0	0	1	0

ECE666/Koren Part.6b.15

Alternative Techniques for Partial Product Accumulation

- ◆ Reducing number of levels in tree - speeding up accumulation
- ◆ Achieving more regular design
- ◆ Tree structures usually have irregular interconnects
 - * Irregularity complicates implementation- area-inefficient layouts
- ◆ Number of tree levels can be lowered by using reduction rate higher than 3:2
- ◆ Achieve 2:1 reduction rate by using SD adders
 - * SD adder also generates sum in constant time
 - * Number of levels in SD adder tree is smaller
 - * Tree produces a single result rather than two for CSA tree

ECE666/Koren Part.6b.16

Copyright 2010 Koren

Final Result of SD Tree


- ◆ In most cases, conversion to two's complement needed
- ◆ Conversion done by forming two sequences:
- ◆ First - Z^+ - created by replacing each negative digit of SD number by 0
- ◆ Second - Z^- - replaces each negative digit with its absolute value, and each positive digit by 0
- ◆ Difference $Z^+ - Z^-$ - found by adding two's complement of Z^- to Z^+ using a CPA
- ◆ Final stage of a CPA needed as in CSA tree

SD Adder Tree vs. CSA Tree

- ◆ SD - no need for a sign bit extension when negative partial products - no separate sign bit
- ◆ Design of SD adder more complex - more gates and larger chip area - each signed digit requires two ordinary bits (or multiple-valued logic)
- ◆ Comparison between the two must be made for specific technology
- ◆ Example:
 - * 32x32 Multiplier based on radix-4 modified Booth's algorithm - 16 partial products
 - * CSA tree with 6 levels, SD adder tree with 4 levels
 - * Sophisticated logic design techniques and layout schemes result in less area-consuming implementations

 (4:2) Compressors

- ◆ Same reduction rate of **2:1** achieved without **SD** representations by using **(4:2)** compressors
- ◆ Designed so that **C_{out}** is not a function of **C_{in}** to avoid a ripple-carry effect
- ◆ **(4:2)** compressor may be implemented as a multi-level circuit with a smaller overall delay compared to implementation based on 2 **(3,2)** counters




ECE666/Koren Part. 6b. 19

Copyright 2010 Koren

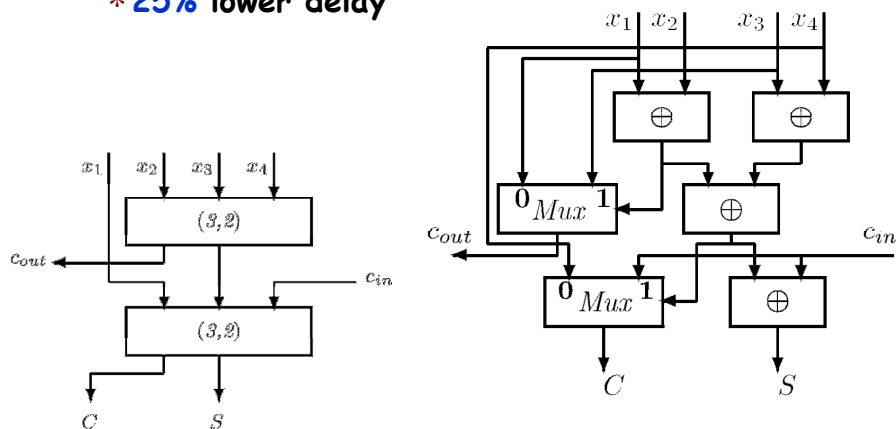Example Implementation

- ◆ Delay of **3** exclusive-or gates to output **S** vs. delay of **4** exclusive-or gates
- * **25%** lower delay



ECE666/Koren Part. 6b. 20

Copyright 2010 Koren

Other Multi-Level Implementations of a (4:2) Compressor

- ◆ All implementations must satisfy

$$x_1 + x_2 + x_3 + x_4 + c_{in} = S + 2(C + c_{out})$$

- ◆ **C_{out}** should not depend on **C_{in}** to avoid horizontal rippling of carries

- ◆ Truth table : (**a,b,c,d,e,f** - Boolean variables)

x_1	x_2	x_3	x_4	c_{out}	C	S	x_1	x_2	x_3	x_4	c_{out}	C	S
0	0	0	0	0	0	c_{in}	1	0	0	0	0	c_{in}	$\overline{c_{in}}$
0	0	0	1	0	c_{in}	$\overline{c_{in}}$	1	0	0	1	d	\overline{d}	c_{in}
0	0	1	0	0	c_{in}	$\overline{c_{in}}$	1	0	1	0	e	\overline{e}	c_{in}
0	0	1	1	a	\overline{a}	c_{in}	1	0	1	1	1	c_{in}	$\overline{c_{in}}$
0	1	0	0	0	c_{in}	$\overline{c_{in}}$	1	1	0	0	f	\overline{f}	c_{in}
0	1	0	1	b	\overline{b}	c_{in}	1	1	0	1	1	c_{in}	$\overline{c_{in}}$
0	1	1	0	c	\overline{c}	c_{in}	1	1	1	0	1	c_{in}	$\overline{c_{in}}$
0	1	1	1	1	c_{in}	$\overline{c_{in}}$	1	1	1	1	1	1	c_{in}

- ◆ Previous implementation - **a=b=c=1, d=e=f=0**

ECE666/Koren Part. 6b. 21

Copyright 2010 Koren

Comparing Delay of Trees

Number of operands	Number of levels using (3,2)	Number of levels using (4;2)	Equivalent delay
3	1	1	1.5
4	2	1	1.5
5 - 6	3	2	3
7 - 8	4	2	3
9	4	3	4.5
10 - 13	5	3	4.5
14 - 16	6	3	4.5
17 - 19	6	4	6
20 - 28	7	4	6
29 - 32	8	4	6
33 - 42	8	5	7.5

ECE666/Koren Part. 6b. 22


Copyright 2010 Koren

Other Implementations

- ◆ Other counters and compressors can be used: e.g., (7,3) counters
- ◆ Other techniques suggested to modify CSA trees which use (3,2) counters to achieve a more regular and less area-consuming layout
- ◆ Such modified tree structures may require a somewhat larger number of CSA levels with a larger overall delay
- ◆ Two such techniques are:
 - * Balanced delay trees
 - * Overturned-stairs trees

ECE666/Koren Part. 6b.23

Copyright 2010 Koren

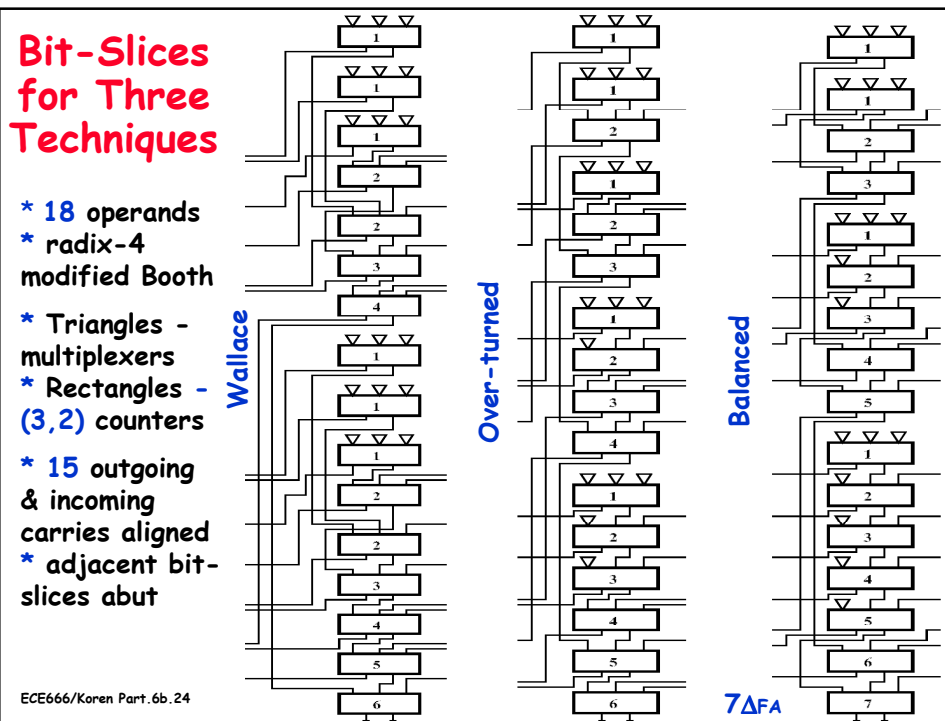


Comparing the Three Trees

- ◆ Incoming carries routed so that all inputs to a counter are valid before or at necessary time
- ◆ Only for **balanced tree** - all 15 incoming carries generated exactly when required - all paths balanced
- ◆ In other 2 - there are counters for which not all incoming carries are generated simultaneously
 - * For example, bottom counter in **overturned-stairs** - incoming carries with delays of $4\Delta FA$ and $5\Delta FA$
- ◆ Number of wiring tracks between adjacent bit-slices (affect layout area)
 - * **Wallace tree** requires 6; **overturned-stairs** 3; **balanced tree** 2 tracks
- ◆ Tradeoff between size and speed
 - * **Wallace** : lowest delay but highest number of wiring tracks
 - * **Balanced**: smallest number of wiring tracks but highest delay

ECE666/Koren Part.6b.25

Copyright 2010 Koren

Complete Structure of Wallace Tree

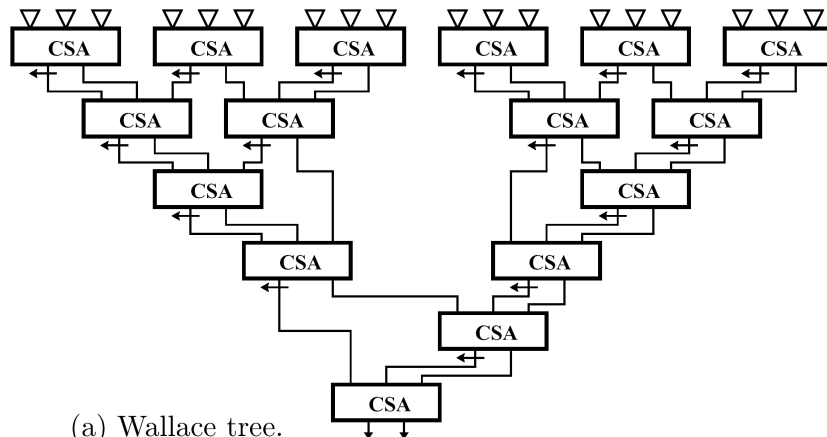


- ◆ **Balanced and overturned-stairs** have regular structure - can be designed in a systematic way

ECE666/Koren Part.6b.26

Copyright 2010 Koren

Complete Structure of Over-turned Tree

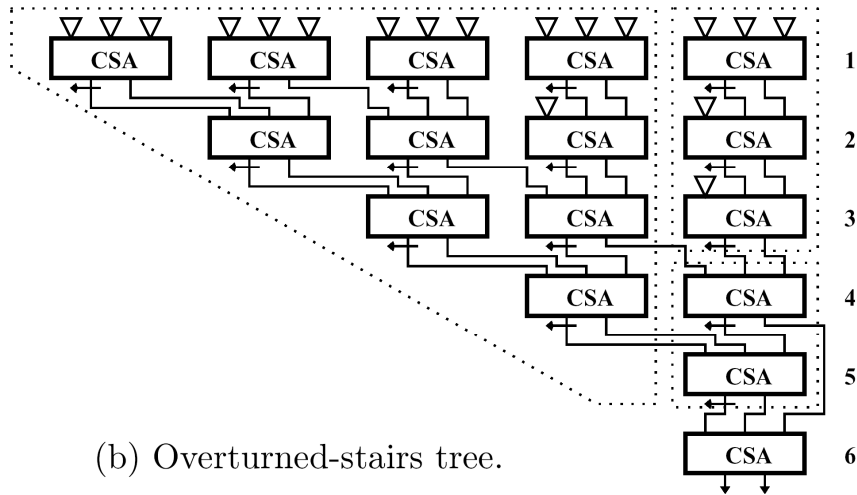


◆ Building blocks indicated with dotted lines

ECE666/Koren Part. 6b. 27

Copyright 2010 Koren

Complete Structure of Balanced Tree

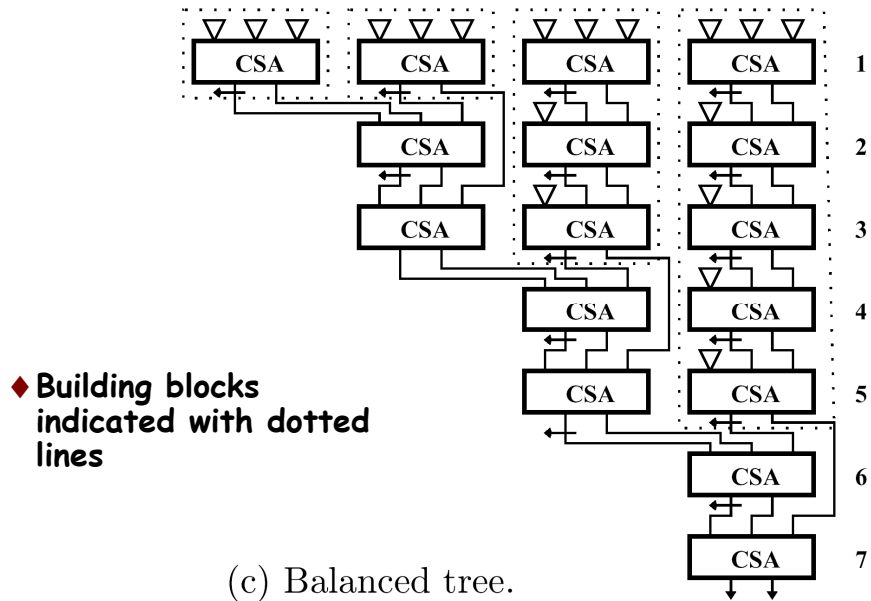


ECE666/Koren Part. 6b. 28

Copyright 2010 Koren

Layout of CSA Tree

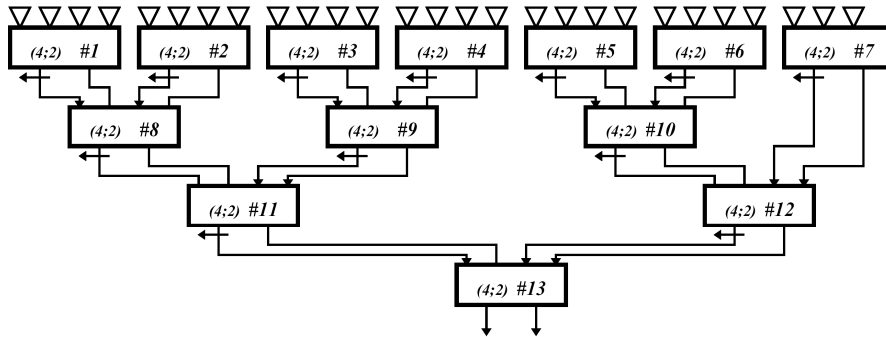- ◆ Wires connecting carry-save adders should have roughly same length for balanced paths
- ◆ CSA tree for 27 operands constructed of (4:2) compressors




ECE666/Koren Part. 6b. 29


Copyright 2010 Koren

Layout of CSA Tree

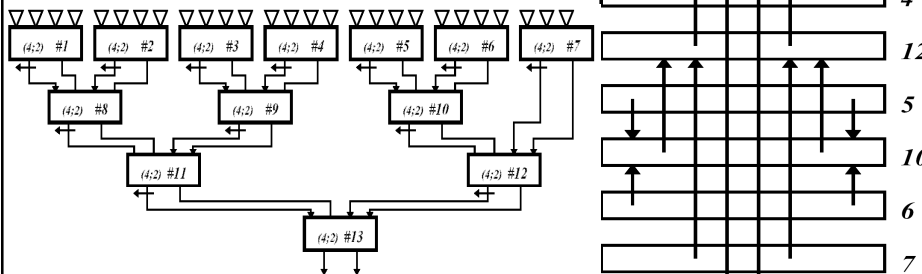- ◆ Bottom compressor (#13) is located in middle so that compressors #11 and #12 are roughly at same distance from it
- ◆ Compressor #11 has equal length wires from #8 and #9



ECE666/Koren Part. 6b. 30

 

Fused Multiply-Add Unit


- ◆ Performs $A \times B$ followed by adding C
 - * $A \times B + C$ done as single and indivisible operation
- ◆ Multiply only: set $C=0$; add (subtract) only: set $B=1$
 - * Can reduce overall execution time of chained multiply and then add/subtract operations
- ◆ **Example:** Evaluation of a polynomial $a_n x^n + a_{n-1} x^{n-1} + \dots + a_0$ through $[(a_n x + a_{n-1})x + a_{n-2}]x + \dots$
- ◆ Independent multiply and add operations can not be performed in parallel
- ◆ Another advantage for floating-point operations - rounding performed only once for $A \times B + C$ rather than twice for multiply and add
 - * Rounding introduces computation errors - reducing number of roundings reduces overall error

ECE666/Koren Part. 6b. 31

Copyright 2010 Koren

Implementing Fused Multiply-Add Unit

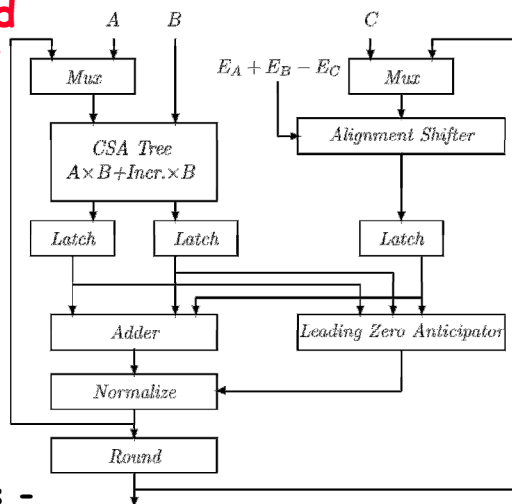- ◆ A, B, C - significands; E_A, E_B, E_C - exponents of operands
- ◆ **CSA** tree generates partial products and performs carry-save accumulation to produce 2 results which are added with properly aligned C
- ◆ Adder gets 3 operands - first reduces to 2 ((3,2) counters), then performs carry-propagate addition
- ◆ Post-normalization and rounding executed next



ECE666/Koren Part. 6b. 32

Copyright 2010 Koren


Two Techniques to reduce Execution Time

- ◆ First: leading zero anticipator circuit uses propagate and generate signals produced by adder to predict type of shift needed in post-normalization step
- ◆ It operates in parallel to addition so that the delay of normalization step is shorter
- ◆ Second (more important): alignment of significand C in $E_A + E_B - E_C$ done in parallel to multiplication
- ◆ Normally, align significand of smaller operand (smaller exponent)
- ◆ Implying: if $A \times B$ smaller than C , have to shift product after generation - additional delay


Instead - Always align C

- ◆ Even if larger than $A \times B$ - allow shift to be performed in parallel to multiplication
- ◆ Must allow C to shift either to right (traditional) or left
- ◆ Direction - $E_A + E_B - E_C$ is positive or negative
- ◆ If C shifted to left - must increase total number of bits in adder

Example

 

 - ◆ Long IEEE operands - possible range of C relative to $A \times B$:



- ◆ $53 \geq E_A + E_B - E_C \geq -53$
- ◆ If $E_A + E_B - E_C \geq 54$, bits of C shifted further to right will be replaced by a sticky bit, and if $E_A + E_B - E_C \leq -54$, all bits of $A \times B$ replaced by sticky bit
- ◆ Overall penalty - 50% increase in width of adder - increasing execution time
- ◆ Top 53 bits of adder need only be capable of incrementing if a carry propagates from lower 106 bits

Additional Computation Paths

- ◆ Path from Round to multiplexer on right used for $(X \times Y + Z) + A \times B$
- ◆ Path from Normalize to multiplexer on left used for $(X \times Y + Z) \times B + C$
- ◆ Rounding step for $(X \times Y + Z)$ is performed at same time as multiplication by B , by adding partial product $\text{Incr.} \times B$ to CSA tree

