



UNIVERSITY OF MASSACHUSETTS
Dept. of Electrical & Computer Engineering

Digital Computer Arithmetic
ECE 666

Part 7c
Fast Division - III

Israel Koren

ECE666/Koren Part.7c.1

Copyright 2010 Koren

Speeding Up the Division Process


- ◆ Unlike multiplication - steps of division are serial
- ◆ Division step consists of selecting quotient digit and calculating new partial remainder
- ◆ Two ways to speed up division:
- ◆ (1) Overlapping full-precision calculation of partial remainder in step i with selecting quotient digit in step $i+1$
 - * Possible since not all bits of new partial remainder must be known to select next quotient digit
- ◆ (2) Replacing carry-propagate add/subtract operation for calculating new partial remainder by carry-save operation

ECE666/Koren Part.7c.2

Copyright 2010 Koren

First Speed-Up Method


- ◆ Truncated approximation of new partial remainder calculated in parallel to full-precision calculation of partial remainder - can be done at high speed
 - * Quotient digit determined before current step completed
- ◆ Instead of: (1) Calculate r_{i-1} (with carry propagation) in step $i-1$ & (2) input N_P most significant bits to PLA to determine q_i
- ◆ Use a small adder with inputs: most significant bits of previous partial remainder, $\widehat{\beta r_{i-2}}$, and most significant bits of corresponding multiple of divisor, $\widehat{q_{i-1}D}$
- ◆ Approximate Partial Remainder (APR) adder

 

ECE666/Koren Part.7c.3

Approximate Partial Remainder Adder

- ◆ Produces approximation of N_P most significant bits of partial remainder, $\widehat{r_{i-1}}$, before full-precision add/sub operation ($r_{i-1} = \beta r_{i-2} - q_{i-1}D$) is completed
- ◆ Allows to perform look-ahead selection of q_i in parallel with calculation of r_{i-1}
- ◆ Size of APR adder determined so that sufficiently accurate N_P bits generated
- ◆ Uncertainty in result of this adder larger than of truncated previous partial remainder $\widehat{\beta r_{i-2}}$ - may need additional inputs for quotient look-up table
- ◆ 8-bit APR adder sufficient to generate necessary inputs to PLA for $\beta=4, \alpha=2$

 


ECE666/Koren Part.7c.4

Copyright 2010 Koren

 **Example:
P-D Plot
($\beta=4, \alpha=2$)
 $D \in [1, 2)$**


- * Horizontal lines determined to reduce complexity of PLA
- * Only 3 divisor bits needed as PLA inputs - most significant bit of divisor always 1
- * For partial remainder - 5 bits (including sign bit) sufficient in most cases




ECE666/Koren Part.7c.5

Positive Remainder

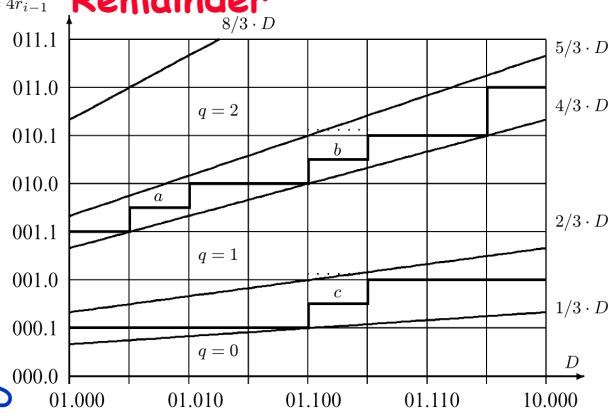- ◆ 3 cases (a,b,c) when additional bit required
- ◆ Case a: $D=1.001$, $P=1.1$ - single fractional bit of P insufficient
- ◆ Divisor can assume any value from 1.001 to 1.010
- ◆ Partial remainder can have a value from 1.1 to 10.0 - range for P/D from $1.1/1.010=1.2$ to $10.0/1.001=1.77$



 - ◆ First requires $q=1$, while second requires $q=2$
- ◆ Add 2nd fractional bit to P
 - * Can select $q=1$ for $P=1.10$ and $q=2$ for $P=1.11$



ECE666/Koren Part.7c.6

Cases b and c

◆ 8-bit APR adder may introduce additional error - increasing P/D range


◆ Case b: $D=1.100$, $P=10.0$

◆ No APR adder: P/D range from $10.0/1.101=1.23$ to $10.1/1.100=1.66$ - $q=1$ can be selected

◆ 8-bit APR adder: introduces error of up to 2^{-6} in r_{i-1} - increases to 2^{-4} after multiplying by 4

◆ This additional error increases maximum value of P/D from 1.66 to 1.7, requiring $q=2$

 ◆ An extra fractional bit of P solves this problem




ECE666/Koren Part.7c.7

Copyright 2010 Koren

Negative Partial Remainder

◆ Represented in two's complement

 ◆ 6 cases - 1 or even 2 additional output bits of APR adder required to guarantee correct selection of quotient digit



ECE666/Koren Part.7c.8

Copyright 2010 Koren

Second Speed-Up Method


- ◆ In first method - time needed for division step determined by add/subtract for remainder - quotient digit selected in previous step
- ◆ Second method avoids time-consuming carry propagation when calculating remainder
- ◆ Truncated remainder sufficient for selecting next quotient digit - no need to complete calculation of remainder at any intermediate step
- ◆ Replace carry-propagate adder by carry-save adder
 - * Partial remainder in a redundant form using 2 sequences of intermediate sum and carry bits (stored in 2 registers)
- ◆ Only most significant sum and carry bits must be assimilated using APR adder to generate approximate remainder and allow selection of quotient digit

ECE666/Koren Part.7c.9

Copyright 2010 Koren

SRT Divider with Redundant Remainder

- ◆ Most time consuming - calculate approximate remainder and select quotient digit
- ◆ In each division step: carry-save adder calculates remainder, APR adder accepts most significant sum and carry bits of remainder & generates required inputs to quotient selection PLA
- ◆ As in first method - number of PLA inputs and its entries need to be calculated, taking into account uncertainty in sum and carry bits representing truncated remainder

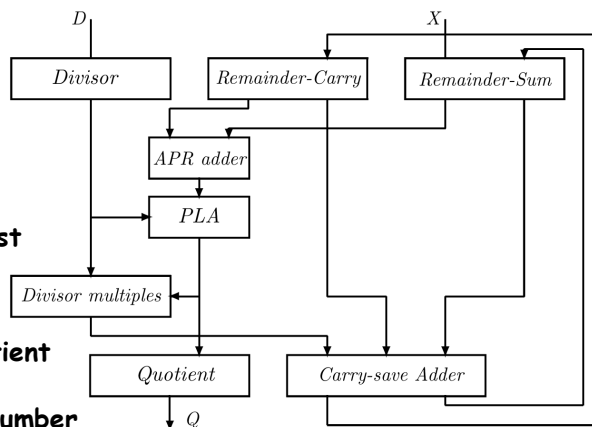

ECE666/Koren Part.7c.10

Copyright 2010 Koren

Example


- ◆ An algorithm for high-speed division with $\beta=4$, $\alpha=2$, $D \in [1,2)$ has been implemented
- ◆ Partial remainder calculated in carry-save manner resulting in a somewhat more complex design
- ◆ 8-bit APR adder used to generate most significant remainder bits - inputs to quotient selection PLA
- ◆ Inputs to APR adder: 8 most significant sum bits and carry bits in redundant representation of remainder
- ◆ Outputs of APR adder converted to a sign-magnitude representation - only 4 bits of approximate partial remainder needed in most cases
- ◆ Additional bit required only in 4 cases - simple PLA

Further Speed-up of SRT Division

- ◆ Achieved by increasing radix β to 8 or higher
- ◆ Reduces number of steps to $\lceil n/3 \rceil$ or lower
- ◆ Several radix-8 SRT dividers have been implemented
- ◆ Main disadvantage: high complexity of PLA - most time-consuming unit of divider
- ◆ Avoiding complex PLA - implementing radix- 2^m SRT unit as a set of m overlapping radix-2 SRT stages
- ◆ Radix-2 SRT requires very simple quotient selection logic - $q_i \in \{-1,0,1\}$ solely determined by remainder - independent of divisor
- ◆ Must overlap quotient selections for m bits - all m quotient bits generated in one step

Two Overlapping Radix-2 SRT Stages

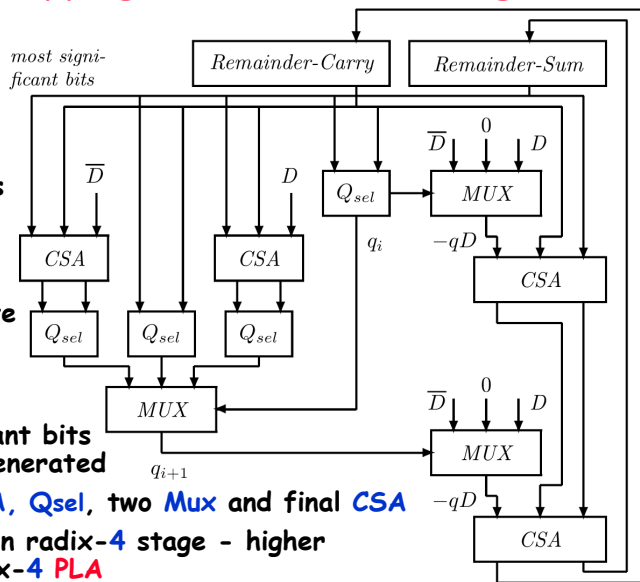- ◆ Implementing radix-4 division
- ◆ All 3 possible values of q_{i+1} generated using 3 Q_{sel} units - correspond to 3 possible intermediate remainders: $2r_{i-1}-D$, $2r_{i-1}$, $2r_{i-1}+D$
- ◆ Only most significant bits of 3 remainders generated
- ◆ Overall delay: CSA, Q_{sel} , two Mux and final CSA
- ◆ May be faster than radix-4 stage - higher complexity of radix-4 PLA



ECE666/Koren Part.7c.13

Copyright 2010 Koren

Extending to Radix-8 SRT division

- ◆ More complex quotient selection circuit - 3 quotient digits (q_i, q_{i+1}, q_{i+2}) generated in parallel
- ◆ For q_{i+1} : calculate speculative remainders $2r_{i-1}-D, 2r_{i-1}, 2r_{i-1}+D$
- ◆ For q_{i+2} : calculate $4r_{i-1}-3D, 4r_{i-1}-2D, 4r_{i-1}-D, 4r_{i-1}, 4r_{i-1}+D, 4r_{i-1}+2D, 4r_{i-1}+3D$
 - * Only most significant bits of these 7 remainders
- ◆ 7 Q_{sel} units required with multiplexors (controlled by q_i and q_{i+1}) to select correct value of q_{i+2}
- ◆ Extend to 4 overlapping radix-2 stages for radix-16 divider: number of Q_{sel} units increases from 11 to 26
- ◆ Another alternative for a radix-16 divider: 2 overlapping radix-4 SRT stages

ECE666/Koren Part.7c.14

Copyright 2010 Koren

Array Dividers


- ◆ All division algorithms can be implemented using arrays: n rows with n cells per row for radix-2 division
- ◆ **Restoring**: each row forms difference between previous remainder and divisor and generates quotient bit according to sign of difference
- ◆ No need to restore remainder if quotient bit=0 - either previous remainder or difference transferred to next row
- ◆ If ripple-carry in every row - n steps to propagate carry in a single row - total execution time of order n^2
- ◆ **Nonrestoring array**: same speed as restoring; only advantage - handle negative operands in a simple way
- ◆ Final remainder may be incorrect - sign opposite to dividend

ECE666/Koren Part.7c.15

Copyright 2010 Koren

A Non-restoring Array Divider

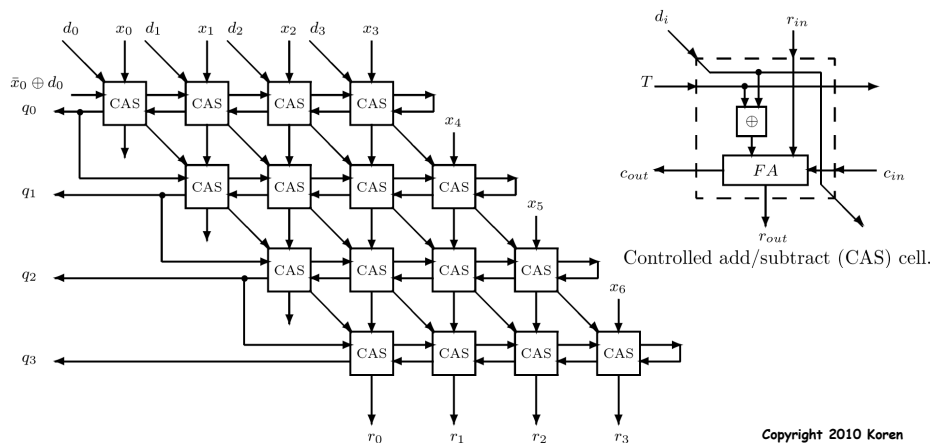If $T=0$ (1) - addition (subtraction) performed;
 Subtract - add two's complement of divisor (assumed positive) & forced carry= T



Copyright 2010 Koren

Faster Array Dividers

- ◆ Previous array dividers - add/subtract with carry-propagation performed in each row
- ◆ **Nonrestoring:**
 - * Only sign bit of partial remainder needed to select quotient bit
 - * Can be generated by using fast carry-look-ahead circuit
 - * Other bits of remainder use carry-save adder
- ◆ Each cell generates P_i and G_i besides sum and carry
- ◆ P_i and G_i of all cells in a row connected to a carry-look-ahead circuit to generate quotient bit
- ◆ Execution time - of order $n \log n$ vs. n^2
- ◆ Similarly, high-radix division array with carry-save addition
- ◆ Small carry-look-ahead adder used to determine most significant bits of remainder to select quotient digit

ECE666/Koren Part.7c.17

Copyright 2010 Koren

Fast Square Root Extraction

- ◆ Similar to division - small extensions to division unit
- ◆ **Nonrestoring** algorithm -
 $q_i = \overline{1, 1}$; $Q = 0.q_1, \dots, q_m$ - calculated square root
- ◆ Advantages of adding 0 to the digit set of q_i :
 - * Shift-only operation required when $q_i = 0$
 - * Overlap between regions of r_i where $q_i = 1$ or $q_i = 0$ are selected leads to reduced precision inspection of remainder
- ◆ Nonrestoring - must identify $r_i \geq 0$ to correctly set q_i
 - * Requires precise determination of sign bit of r_i
- ◆ If $q_i = 0$ allowed - lower precision comparison sufficient, enables use of carry-save adders for r_i
- ◆ Remainder: two sequences - partial sum and carries
- ◆ Only a few high-order bits of these two sequences must be examined to select q_i

ECE666/Koren Part.7c.18

Copyright 2010 Koren

Selection of $q_i=0$

- ◆ Square root Q restricted to normalized fraction - $1/2 \leq Q < 1$, with $q_1=1$
- ◆ Radicand: $1/4 \leq X < 1$
- ◆ Remainder r_{i-1} ($i \geq 2$): $-2(Q_{i-1}-2^{-i}) \leq r_{i-1} \leq 2(Q_{i-1}+2^{-i})$
(Q_{i-1} is partially calculated root at step $i-1$ -
 $Q_{i-1}=0.q_1q_2\dots q_{i-1}$)
- ◆ In step $i \geq 2$, select $q_i=0$ whenever r_{i-1} is in range
 $[-(Q_{i-1} - 2^{-i-1}), (Q_{i-1} + 2^{-i-1})]$
- ◆ If $q_i=0$, $r_i=2r_{i-1}$

Selection Rule for q_i

$$q_i = \begin{cases} 1 & \text{if } r_{i-1} \geq (Q_{i-1} + 2^{-i-1}) \\ 0 & \text{if } -(Q_{i-1} - 2^{-i-1}) \leq r_{i-1} \leq (Q_{i-1} + 2^{-i-1}) \\ \bar{1} & \text{if } r_{i-1} \leq -(Q_{i-1} - 2^{-i-1}). \end{cases}$$

- ◆ Since $Q_{i-1} + 2^{-i-1}$ and $Q_{i-1} - 2^{-i-1}$ are in $[1/2, 1]$, a selection rule which avoids a high-precision comparison is

$$q_i = \begin{cases} 1 & \text{if } 1/2 \leq 2r_{i-1} \leq 2 \\ 0 & \text{if } -1/2 \leq 2r_{i-1} < 1/2 \\ \bar{1} & \text{if } -2 \leq 2r_{i-1} < -1/2. \end{cases}$$

- ◆ Similar to the **SRT** rule

Example

◆ $X = .0111101_2 = 61/128$

$r_0 = X$		0.0111101	
$2r_0$		0.1111010	set $q_1 = 1, Q_1 = 0.1$
$-(0 + 2^{-1})$	-	0.1000000	
r_1		0.0111010	
$2r_1$		0.1110100	set $q_2 = 1, Q_2 = 0.11$
$-(2Q_1 + 2^{-2})$	- 0	1.0100000	
r_2		1.1010100	
$2r_2$	1	1.0101000	set $q_3 = \bar{1}, Q_3 = 0.101$
$+(2Q_2 - 2^{-3})$	+ 0	1.0110000	
r_3		0.1011000	
$2r_3$		0.1011000	set $q_4 = 1, Q_4 = 0.1011$
$-(2Q_3 + 2^{-4})$	- 0	1.0101000	
r_4		0.0001000	
$2r_4$		0.0010000	set $q_5 = 0, Q_5 = 0.10110$
r_5		0.0010000	
$2r_5$		0.0100000	set $q_6 = 0, Q_6 = 0.101100$
r_6		0.0100000	
$2r_6$		0.1000000	set $q_7 = 1, Q_7 = 0.1011001$
$-(2Q_6 + 2^{-7})$	- 0	1.0110001	
r_7	1	0.0001111	

◆ **Square root:**
 $Q = .1011001_2 = 89/128$

◆ **Final remainder:**
 $2^{-7} r_7 = -113/2^{14} = X - Q^2 = (7808-7921)/2^{14}$

ECE666/Koren Part.7c.21 Copyright 2010 Koren

High-Radix Square Root Extraction

- ◆ β - radix; digit set for q_i - $\{\bar{\alpha}, \bar{\alpha} - 1, \dots, \bar{1}, 0, 1, \dots, \alpha\}$
- ◆ Computing new remainder: $r_i = \beta r_{i-1} - q_i (2Q_{i-1} + q_i \beta^{-i})$
- ◆ **Example:**
 $\beta=4$, digit set $\{\bar{2}, \bar{1}, 0, 1, 2\}$ preferable - eliminates need to generate multiple $3Q_{i-1}$
- ◆ Generation of $q_i (2Q_{i-1} + q_i 4^{-i})$ makes square root extraction somewhat more complex than division
- ◆ Calculation can be simplified
- ◆ For $q_i=1, 2$ - subtract $Q001_2$ & $Q010_2$, respectively
- ◆ For $q_i=\bar{1}$ - add $Q00\bar{1}_2$ - same as $(Q-1)111_2$
- ◆ For $q_i=\bar{2}$ - add $Q0\bar{1}0_2$ - same as $(Q-1)110_2$
- ◆ Two registers with Q and $Q-1$, updated at every step, simplify execution of square root algorithm

ECE666/Koren Part.7c.22 Copyright 2010 Koren

Selecting Quotient Digit

- ◆ Only low-precision comparison of remainder needed to select quotient digit -
 - * Perform add/subtract in carry-save - small carry-propagate adder to calculate most significant bits of r_i
 - * To provide inputs to a PLA for selecting square root digit q_i
 - * Other inputs to PLA: most significant bits of root multiple
- ◆ Several rules for selecting q_i have been proposed
 - * Intervals of remainder determine size of carry-propagate adder (between 7 and 9 bits for base-4 algorithm with digits 2,1,0,1,2) and exact PLA entries
- ◆ Selected q_i depends on truncated remainder and truncated root multiple
- ◆ In first step no estimated root available
- ◆ Separate PLA for predicting first few bits of root

ECE666/Koren Part.7c.23

Copyright 2010 Koren

Example - Square Root Using Radix-4 Divider

- ◆ P-D plot for divide also used for square root
- ◆ Same PLA (with 19 product terms) used for predicting next quotient digit and root digit
- ◆ A separate PLA (with 28 product terms) added
 - * Inputs - 6 most significant bits of significand and least significant bit of exponent (indicates whether exponent odd or even)
 - * Output - 5 most significant bits of root

$$\sqrt{1.f \cdot 2^{E-1023}} = \begin{cases} \sqrt{0.1f} \cdot 2^{(E+1)/2-1023} & \text{if } E \text{ is odd} \\ \sqrt{0.01f} \cdot 2^{E/2+1-1023} & \text{if } E \text{ is even} \end{cases}$$

- ◆ Radicand in $[1/4, 1] \Rightarrow$ square root in $[1/2, 1]$

ECE666/Koren Part.7c.24

Copyright 2010 Koren